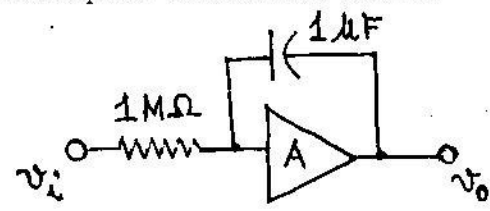


58. Give that the critical field for Al at absolute zero, $H_c(T = 0) = 105.16$ Oe, the stabilization energy of the superconducting state at absolute zero per unit volume of the sample is
- (A) 440 ergs/cm³
 - (B) 250 ergs/cm³
 - (C) 760 ergs/cm³
 - (D) 165 ergs/cm³
59. An *n*-channel FET with donor density 9×10^{15} electrons/cm³ and half the depletion width of 3μ is biased such that $V_{GS} = \frac{1}{2}V_p$ and $I_D = 0$. Given the relative dielectric constant as 12, the channel half width is
- (A) 1μ
 - (B) 0.87μ
 - (C) 0.087μ
 - (D) 8.7μ
60. A full wave rectifier has to supply 100 mA at 350 V with a ripple less than 10 V. For a simple *L*-section filter to do this, the LC product must at least be
- (A) 19 sec
 - (B) 29 sec
 - (C) 39 sec
 - (D) 49 sec

61. The output of the operational amplifier circuit shown below is



- (A) $\int v_i dt$
- (B) $-\frac{dv_i}{dt}$
- (C) $+\frac{dv_i}{dt}$
- (D) $-\int v_i dt$

62. Which of the following is equivalent to the Boolean expression

$$\bar{A}\bar{B}\bar{C} + B\bar{C}\bar{D} + A\bar{B}\bar{C}$$

- (A) $\bar{B}\bar{C} + BD$
- (B) $\bar{C}\bar{B} + \bar{C}\bar{D}$
- (C) $\bar{C}\bar{D} + \bar{C}D$
- (D) $\bar{C}\bar{D} + \bar{B}\bar{C}D$